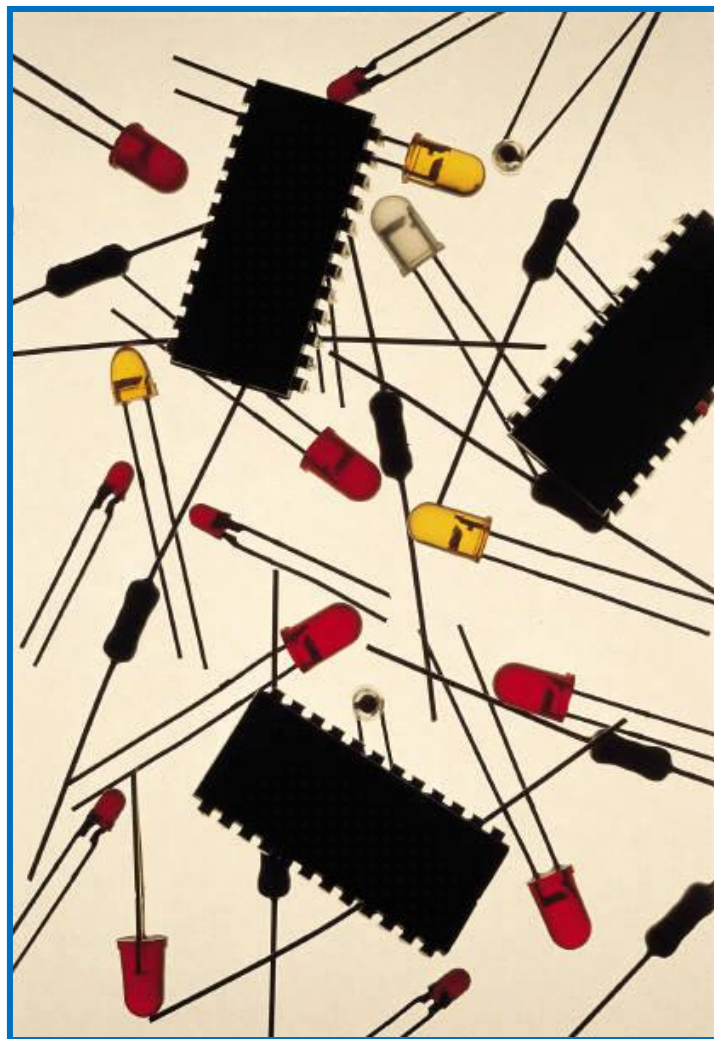


# **ANALOGUE AND DIGITAL ELECTRONICS**

## **Supplementary material: WORKSHEETS**



**Joaquim Crisol**  
**Llicència D, Generalitat de Catalunya**  
**NILE Norwich, April of 2011**

## Table of contents.

Worksheet 1A.....	2
Worksheet 1B.....	3
Summative assessment .....	4

<b>Unit 1, Activity 11</b>	Text underlined is for dictation “A to B”.
----------------------------	--

Signals in nature are analogue. For example, sound is an air pressure wave<sup>(a)</sup>. It is analogue because it can be any value.

\_\_\_\_\_ <sup>(b)</sup>.

- They can be converted to numbers and easily processed by computers<sup>(a)</sup>.
- They are easy to store and to compress using mathematical algorithms.
- Noise \_\_\_\_\_ <sup>(b)</sup> as much as to analogue signals.


When data is transmitted, processed or stored a certain amount of **NOISE** enters into the signal<sup>(a)</sup>.

With an analogue signal, noise cannot \_\_\_\_\_ <sup>(b)</sup>.

We have distortion. In a digital signal, noise will not matter, as any signal close enough to a particular value will be interpreted as that value.

<b>Unit 3, Activity 7</b>	Logic diagram description and solution.
---------------------------	---

Describe this diagram to your partner B.

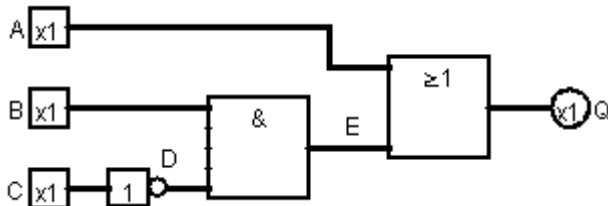

Expression:  $Q = A + B \cdot \overline{C}$

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

<b>Unit 1, Activity 11</b>	Text underlined is for dictation “B to A”.
----------------------------	--

Signals in nature are analogue. For example, \_\_\_\_\_<sup>(a)</sup>. It is analogue because it can be any value.

Digital signals have many advantages<sup>(b)</sup>:


- They can be converted to numbers and easily \_\_\_\_\_<sup>(a)</sup>.
- They are easy to store and to compress using mathematical algorithms.
- Noise does not affect them<sup>(b)</sup> as much as to analogue signals.

When data is transmitted, processed or stored a certain amount of **NOISE** \_\_\_\_\_<sup>(a)</sup>.

With an analogue signal, noise cannot be distinguished from the original signal<sup>(b)</sup>. We have distortion. In a digital signal, noise will not matter, as any signal close enough to a particular value will be interpreted as that value.

<b>Unit 3, Activity 7</b>	Logic diagram description and solution.
---------------------------	---

Describe this diagram to your partner A.

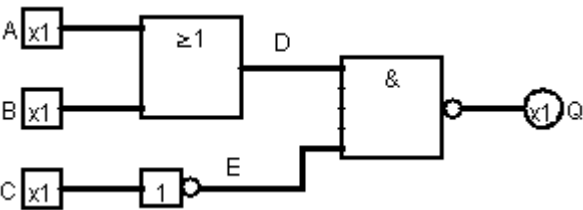


A	B	C	Q
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Expression:  $Q = (A+B) \cdot \overline{C}$

<b>Name:</b>	<b>Group:</b>	_/_/_
--------------	---------------	-------

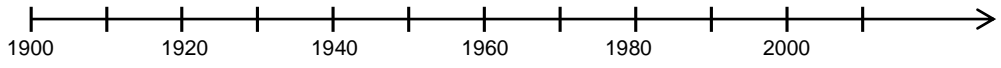**01** a) Place on the time line three main developments in the history of electronics.



b) Underline the right words:

- A fan is an *electrical/electronic* device because it transforms *information/energy*.
- The *process/input/output* part of a thermometer converts temperature into electric signals.
- A *digital/analogue* signal is less affected by noise.
- *Binary/analogue* signals are more difficult to manipulate and store.


c) What is the problem with e-waste? Propose two measures to deal with it.  
E-waste is...

**02** a) What are the colours for a 5k6 (10%) resistor?

Black	0
Brown	1
Red	2
Orange	3
Yellow	4
Green	5
Blue	6
Violet	7
Grey	8
White	9
Silver	10%
Gold	5%

b) Obtain the minimum and maximum value for a resistor with these colours: brown / green / red // silver

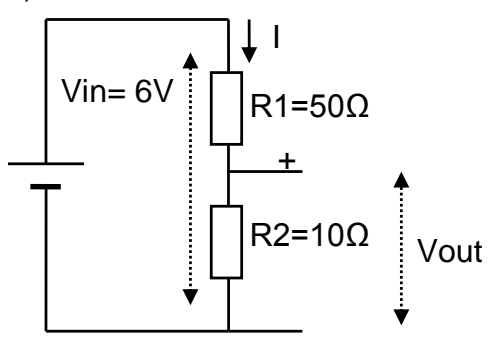c) What do we call this kind of circuit? ..... Calculate  $V_{out}$ .





d) Explain how  $V_o$  will change depending on the temperature if  $R_2$  is a PTC?

If temperature ..... then  $R_2$  will .....

If  $R_2$  .....

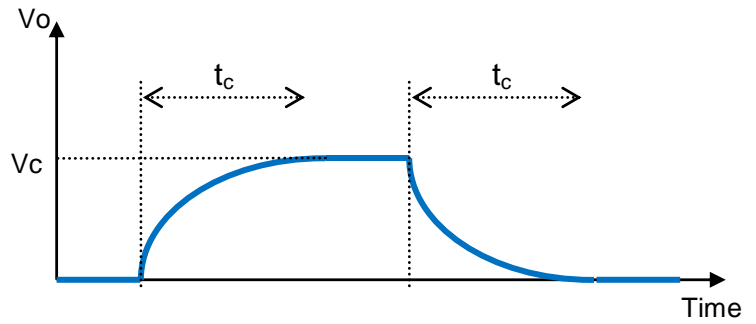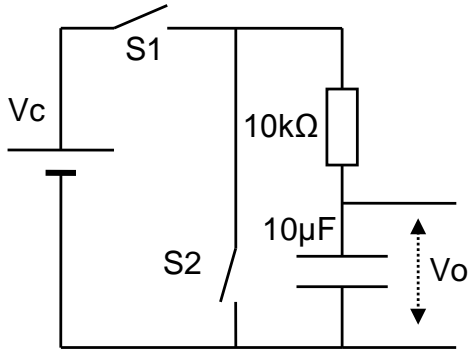**03** a) Calculate the charge and discharge time ( $t_c$ ) for this circuit:





b) Underline the right words:

A transistor/capacitor/diode is a semiconductor device that allows current to flow in one direction. The current can only flow from base/anode to cathode/collector.

A transistor/capacitor is a semiconductor device used to charge/amplify electronic signals. It has two/three terminals for connection to an external circuit.

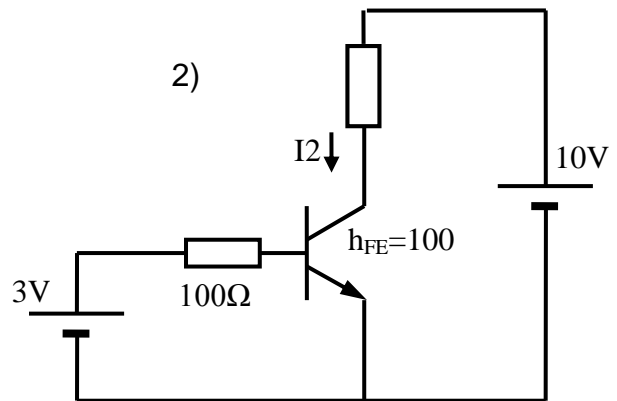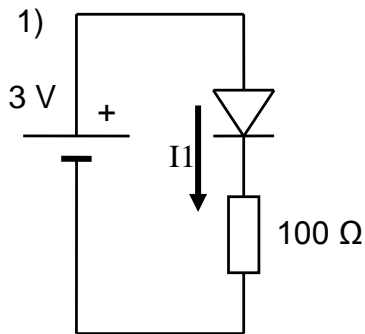c) Calculate the currents in this circuit





04 a) Convert “a” from binary to digital and “b” from digital to binary.


	Binary	Binary weight					Decimal
		16	8	4	2	1	
a)	01110						
b)							5

b) Add them in binary.

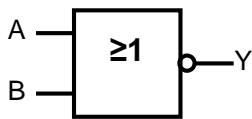c) Identify the type of gates which these diagrams represent.




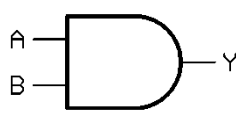

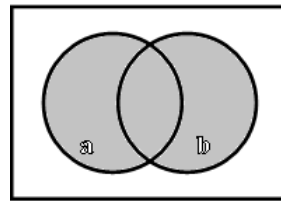


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

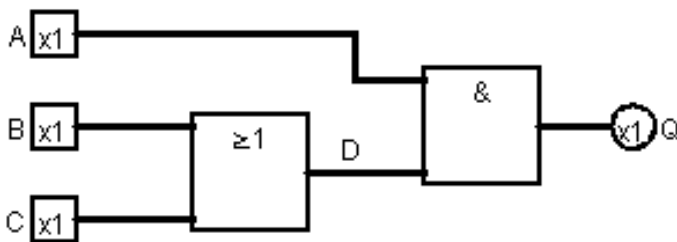05 a) Find the expression for this logic system and fill in the truth table.



Expression:

A	B	C	Q
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

b) Design a logic system for a water supply system. The water pump must be on when the deposit is empty or when the tap is open. Find the expression, the circuit with IEC symbols and the truth table. Circle the combination in which the deposit is empty and the tap closed.

Inputs:

A: deposit (0 empty, 1 full)

B: tap (0 closed, 1 open)

Output:

Q= pump (0 off, 1 on)

Expression:

A	B	Q
0	0	
0	1	
1	0	
1	1	